

Chapter 18, Solution 1.


$$f'(t) = \delta(t+2) - \delta(t+1) - \delta(t-1) + \delta(t-2)$$

$$\begin{aligned} j\omega F(\omega) &= e^{j2\omega} - e^{j\omega} - e^{-j\omega} + e^{-j2\omega} \\ &= 2\cos 2\omega - 2\cos \omega \end{aligned}$$

$$F(\omega) = \frac{2[\cos 2\omega - \cos \omega]}{j\omega}$$

Chapter 18, Solution 2.
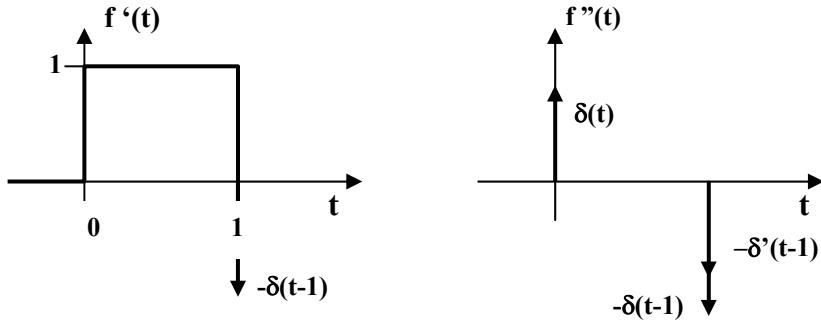
$$f(t) = \begin{cases} t, & 0 < t < 1 \\ 0, & \text{otherwise} \end{cases}$$



$$f''(t) = \delta(t) - \delta(t-1) - \delta'(t-1)$$

Taking the Fourier transform gives

$$-\omega^2 F(\omega) = 1 - e^{-j\omega} - j\omega e^{-j\omega}$$

$$F(\omega) = \frac{(1 + j\omega)e^{-j\omega} - 1}{\omega^2}$$

$$\text{or } F(\omega) = \int_0^1 t e^{-j\omega t} dt$$

$$\text{But } \int x e^{ax} dx = \frac{e^{ax}}{a^2} (ax - 1) + c$$



$$F(\omega) = \frac{e^{-j\omega}}{(-j\omega)^2} (-j\omega t - 1) \Big|_0^1 = \frac{1}{\omega^2} [(1 + j\omega)e^{-j\omega} - 1]$$

Chapter 18, Solution 3.

$$f(t) = \frac{1}{2}t, -2 < t < 2, \quad f'(t) = \frac{1}{2}, -2 < t < 2$$

$$\begin{aligned} F(\omega) &= \int_{-2}^2 \frac{1}{2}t e^{j\omega t} dt = \frac{e^{-j\omega t}}{2(-j\omega)^2} (-j\omega t - 1) \Big|_{-2}^2 \\ &= -\frac{1}{2\omega^2} [e^{-j\omega 2} (-j\omega 2 - 1) - e^{j\omega 2} (j\omega 2 - 1)] \\ &= -\frac{1}{2\omega^2} [-j\omega 2 (e^{j\omega 2} + e^{-j\omega 2}) + e^{j\omega 2} - e^{-j\omega 2}] \\ &= -\frac{1}{2\omega^2} (-j\omega 4 \cos 2\omega + j2 \sin 2\omega) \\ F(\omega) &= \underline{\frac{j}{\omega^2} (\sin 2\omega - 2\omega \cos 2\omega)} \end{aligned}$$

Chapter 18, Solution 4.

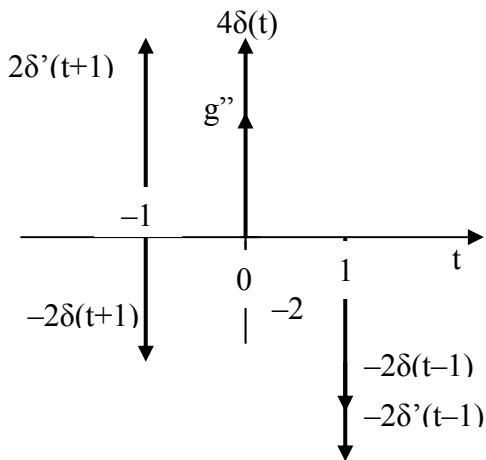
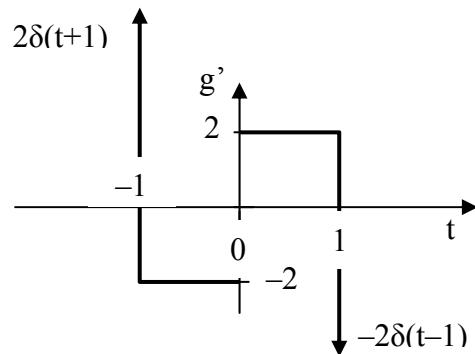


$$g'' = -2\delta(t+1) + 2\delta'(t+1) + 4\delta(t) - 2\delta(t-1) - 2\delta'(t-1)$$

$$\begin{aligned}(j\omega)^2 G(\omega) &= -2e^{j\omega} + 2j\omega e^{j\omega} + 4 - 2e^{-j\omega} - 2j\omega e^{-j\omega} \\ &= -4 \cos \omega - 4\omega \sin \omega + 4\end{aligned}$$

$$G(\omega) = \frac{4}{\omega^2} (\cos \omega + \omega \sin \omega - 1)$$

Chapter 18, Solution 5.

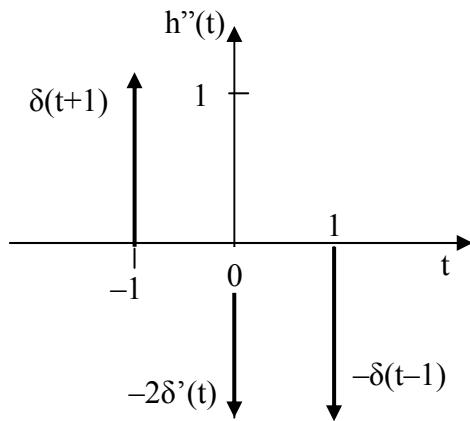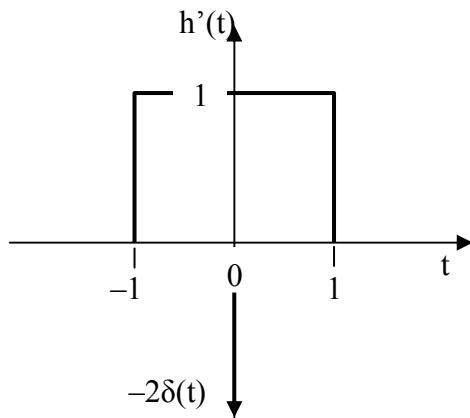

$$h''(t) = \delta(t+1) - \delta(t-1) - 2\delta'(t)$$

$$(j\omega)^2 H(\omega) = e^{j\omega} - e^{-j\omega} - 2j\omega = 2j \sin \omega - 2j\omega$$

$$H(\omega) = \frac{2j}{\omega} - \frac{2j}{\omega^2} \sin \omega$$

Chapter 18, Solution 6.

$$F(\omega) = \int_{-1}^0 (-1)e^{-j\omega t} dt + \int_0^1 te^{-j\omega t} dt$$

$$\begin{aligned} \operatorname{Re} F(\omega) &= - \int_{-1}^0 \cos \omega t dt + \int_0^1 t \cos \omega t dt \\ &= -\frac{1}{\omega} \sin \omega t \Big|_{-1}^0 + \left(\frac{1}{\omega^2} \cos \omega t + \frac{t}{\omega} \sin \omega t \right) \Big|_0^1 = \frac{1}{\omega^2} (\cos \omega - 1) \end{aligned}$$

Chapter 18, Solution 7.

(a) f_1 is similar to the function $f(t)$ in Fig. 17.6.

$$f_1(t) = f(t-1)$$

$$\text{Since } F(\omega) = \frac{2(\cos \omega - 1)}{j\omega}$$

$$F_1(\omega) = e^{j\omega} F(\omega) = \frac{2e^{-j\omega}(\cos \omega - 1)}{j\omega}$$

Alternatively,

$$\begin{aligned} f_1'(t) &= \delta(t) - 2\delta(t-1) + \delta(t-2) \\ j\omega F_1(\omega) &= 1 - 2e^{-j\omega} + e^{-j2\omega} = e^{-j\omega}(e^{j\omega} - 2 + e^{j\omega}) \\ &= e^{-j\omega}(2 \cos \omega - 2) \end{aligned}$$

$$F_1(\omega) = \frac{2e^{-j\omega}(\cos \omega - 1)}{j\omega}$$

(b) f_2 is similar to $f(t)$ in Fig. 17.14.
 $f_2(t) = 2f(t)$

$$F_2(\omega) = \frac{4(1 - \cos \omega)}{\omega^2}$$

$$= \frac{5e^{-j2t}}{2-j2} + \frac{5e^{+j2t}}{2+j2} = \frac{5}{2\sqrt{2}} [e^{-j(2t-45^\circ)} + e^{j(2t-45^\circ)}]$$

$$= \frac{5}{\sqrt{2}} \cos(2t - 45^\circ)$$

$$v_o(2) = \frac{5}{\sqrt{2}} \cos(4 - 45^\circ) = \frac{5}{\sqrt{2}} \cos(229.18^\circ - 45^\circ)$$

$$v_o(2) = \underline{-3.526 \text{ V}}$$

Chapter 18, Solution 37.

$$2 \parallel j\omega = \frac{j2\omega}{2 + j\omega}$$

By current division,

$$H(\omega) = \frac{I_o(\omega)}{I_s(\omega)} = \frac{\frac{j2\omega}{2 + j\omega}}{4 + \frac{j2\omega}{2 + j\omega}} = \frac{j2\omega}{j2\omega + 8 + j4\omega}$$

$$H(\omega) = \underline{\frac{j\omega}{4 + j3\omega}}$$

Chapter 18, Solution 38.

$$V_i(\omega) = \pi\delta(\omega) + \frac{1}{j\omega}$$

$$V_o(\omega) = \frac{10}{10 + j\omega 2} V_i(\omega) = \frac{5}{5 + j\omega} \left(\pi\delta(\omega) + \frac{1}{j\omega} \right)$$

$$\text{Let } V_o(\omega) = V_1(\omega) + V_2(\omega) = \frac{5\pi\delta(\omega)}{5 + j\omega} + \frac{5}{j\omega(5 + j\omega)}$$

$$V_2(\omega) = \frac{5}{s(s+5)} = \frac{A}{s} + \frac{B}{s+5} \longrightarrow A = 1, B = -1, s = j\omega$$

$$V_2(\omega) = \frac{1}{j\omega} - \frac{1}{5+j\omega} \longrightarrow v_2(t) = \frac{1}{2} \operatorname{sgn}(t) - e^{-5t}$$

$$V_1 = \frac{5\pi\delta(\omega)}{5+j\omega} \longrightarrow v_1(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \frac{5\pi\delta(\omega)}{5+j\omega} e^{j\omega t} d\omega$$

$$v_1(t) = \frac{5\pi}{2\pi} \cdot \frac{1}{5} = 0.5$$

$$v_o(t) = v_1(t) + v_2(t) = 0.5 + 0.5 \operatorname{sgn}(t) - e^{-5t}$$

$$\text{But } \operatorname{sgn}(t) = -1 + 2u(t)$$

$$v_o(t) = +0.5 - 0.5 + u(t) - e^{-5t}u(t) = \underline{u(t) - e^{-5t}u(t)}$$

Chapter 18, Solution 39.

$$V_s(\omega) = \int_{-\infty}^{\infty} (1-t)e^{-j\omega t} dt = \frac{1}{j\omega} + \frac{1}{\omega^2} - \frac{1}{\omega^2} e^{-j\omega}$$

$$I(\omega) = \frac{V_s(\omega)}{10^3 + j\omega \times 10^{-3}} = \frac{10^3}{10^6 + j\omega} \left(\frac{1}{j\omega} + \frac{1}{\omega^2} - \frac{1}{\omega^2} e^{-j\omega} \right)$$

Chapter 18, Solution 40.

$$\ddot{v}(t) = \delta(t) - 2\delta(t-1) + \delta(t-2)$$

$$-\omega^2 V(\omega) = 1 - 2e^{-j\omega} + e^{j\omega 2}$$

$$V(\omega) = \frac{1 - 2e^{-j\omega} + e^{-j\omega 2}}{-\omega^2}$$

$$\text{Now } Z(\omega) = 2 + \frac{1}{j\omega} = \frac{1 + j2\omega}{j\omega}$$

$$I = \frac{V(\omega)}{Z(\omega)} = \frac{2e^{j\omega} - e^{j\omega^2} - 1}{\omega^2} \cdot \frac{j\omega}{1 + j2\omega}$$


$$= \frac{1}{j\omega(0.5 + j\omega)} (0.5 + 0.5e^{-j\omega^2} - e^{-j\omega})$$

But $\frac{1}{s(s+0.5)} = \frac{A}{s} + \frac{B}{s+0.5} \longrightarrow A = 2, B = -2$

$$I(\omega) = \frac{2}{j\omega} (0.5 + 0.5e^{j\omega^2} - e^{-j\omega}) - \frac{2}{0.5 + j\omega} (0.5 + 0.5e^{-j\omega^2} - e^{-j\omega})$$

$$i(t) = \frac{1}{2} \text{sgn}(t) + \frac{1}{2} \text{sgn}(t-2) - \text{sgn}(t-1) - e^{-0.5t} u(t) - e^{-0.5(t-2)} u(t-2) - 2e^{-0.5(t-1)} u(t-1)$$

Chapter 18, Solution 41.

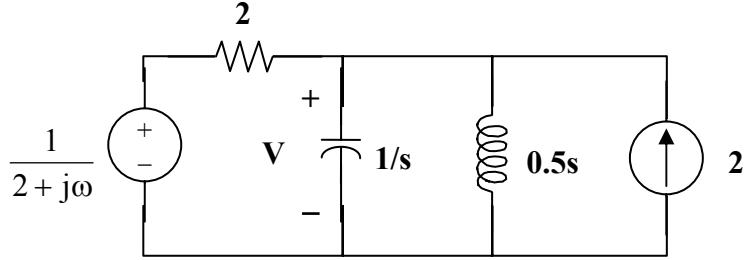

$$V - \frac{1}{2 + j\omega} + j\omega V + \frac{2V}{j\omega} - 2 = 0$$

$$(j\omega - 2\omega^2 + 4)V = j4\omega + \frac{j\omega}{2 + j\omega} = \frac{-4\omega^2 + j9\omega}{2 + j\omega}$$

$$V(\omega) = \frac{2j\omega(4.5 + j2\omega)}{(2 + j\omega)(4 - 2\omega^2 + j\omega)}$$

$$i_o(t) = \frac{2 \operatorname{sgn}(t) - 2 \operatorname{sgn}(t-1) - 4e^{-2t}u(t) + 4e^{-2(t-1)}u(t-1)A}{}$$

Chapter 18, Solution 43.

$$20 \text{ mF} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j20 \times 10^{-3} \omega} = \frac{50}{j\omega}, \quad i_s = 5e^{-t} \longrightarrow I_s = \frac{1}{5 + j\omega}$$

$$V_o = \frac{40}{40 + \frac{50}{j\omega}} I_s \bullet \frac{50}{j\omega} = \frac{50}{(s+1.25)(s+5)}, \quad s = j\omega$$


$$V_o = \frac{A}{s+1.25} + \frac{B}{s+5} = \frac{40}{3} \left[\frac{1}{j\omega + 1.25} - \frac{1}{j\omega + 5} \right]$$

$$v_o(t) = \frac{40}{3} (e^{-1.25t} - e^{-5t}) u(t)$$


Chapter 18, Solution 44.

$$1H \longrightarrow j\omega$$

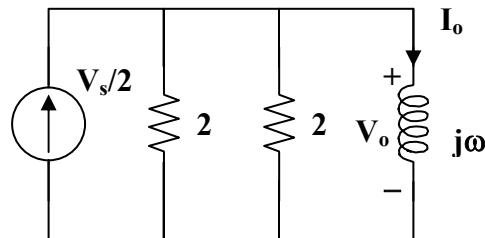We transform the voltage source to a current source as shown in Fig. (a) and then combine the two parallel 2Ω resistors, as shown in Fig. (b).



(a)

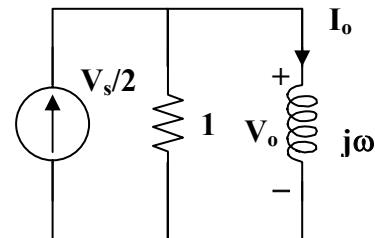

(b)

$$2\parallel 2 = 1\Omega, \quad I_o = \frac{1}{1+j\omega} \cdot \frac{V_s}{2}$$

$$V_o = j\omega I_o = \frac{j\omega V_s}{2(1+j\omega)}$$

$$\ddot{v}_s(t) = 10\delta(t) - 10\delta(t-2)$$

$$j\omega V_s(\omega) = 10 - 10e^{-j2\omega}$$

$$V_s(\omega) = \frac{10(1 - e^{-j2\omega})}{j\omega}$$

Hence $V_o = \frac{5(1 - e^{-j2\omega})}{1 + j\omega} = \frac{5}{1 + j\omega} - \frac{5}{1 + j\omega}e^{-j2\omega}$

$$v_o(t) = 5e^{-t}u(t) - 5e^{-(t-2)}u(t-2)$$

$$v_o(1) = 5e^{-1} - 1 - 0 = \underline{\underline{1.839 \text{ V}}}$$

Chapter 18, Solution 45.

$$V_o = \frac{\frac{1}{j\omega}}{2 + j\omega + \frac{1}{j\omega}}(2) = \frac{2}{(j\omega + 1)^2} \longrightarrow v_o(t) = 2te^{-t}u(t)$$

Chapter 18, Solution 46.


$$\frac{1}{4}F \longrightarrow \frac{1}{j\omega \frac{1}{4}} = \frac{-j4}{\omega}$$

$$2H \longrightarrow j\omega 2$$

$$3\delta(t) \longrightarrow 3$$

$$e^{-t}u(t) \longrightarrow \frac{1}{1 + j\omega}$$

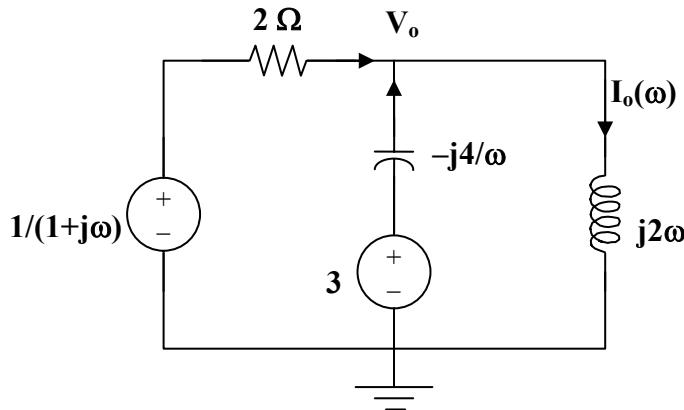The circuit in the frequency domain is shown below:



At node V_o , KCL gives

$$\frac{\frac{1}{1+j\omega} - V_o}{2} + \frac{3 - V_o}{\frac{-j4}{\omega}} = \frac{V_o}{j2\omega}$$

$$\frac{2}{1+j\omega} - 2V_o + j\omega 3 - j\omega V_o = -\frac{j2V_o}{\omega}$$


$$V_o = \frac{\frac{2}{1+j\omega} + j\omega 3}{2 + j\omega - \frac{j2}{\omega}}$$

$$I_o(\omega) = \frac{V_o}{j2\omega} = \frac{\frac{2 + j\omega 3 - 3\omega^2}{1 + j\omega}}{j2\omega \left(2 + j\omega - \frac{j2}{\omega} \right)}$$

$$I_o(\omega) = \frac{2 + j\omega^2 - 3\omega^2}{4 - 6\omega^2 + j(8\omega - 2\omega^3)}$$

Chapter 18, Solution 47.

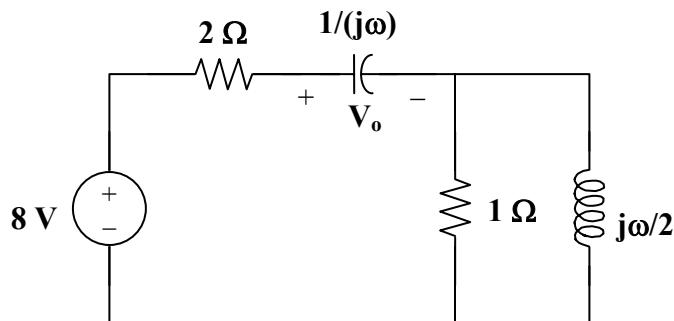Transferring the current source to a voltage source gives the circuit below:



$$\text{Let } Z_{in} = 2 + 1 \parallel \frac{j\omega}{2} = 2 + \frac{\frac{j\omega}{2}}{1 + \frac{j\omega}{2}} = \frac{4 + j3\omega}{2 + j\omega}$$

By voltage division,

$$\begin{aligned} V_o(\omega) &= \frac{\frac{1}{j\omega}}{\frac{1}{j\omega} + Z_{in}} \cdot 8 = \frac{8}{1 + j\omega Z_{in}} = \frac{8}{1 + \frac{j\omega(4 + j3\omega)}{2 + j\omega}} \\ &= \frac{8(2 + j\omega)}{2 + j\omega + j\omega 4 - 3\omega^2} \\ &= \underline{\underline{\frac{8(2 + j\omega)}{2 + j\omega 5 - 3\omega^2}}} \end{aligned}$$

Chapter 18, Solution 48.

$$0.2F \longrightarrow \frac{1}{j\omega C} = -\frac{j5}{\omega}$$

As an integrator,

$$RC = 20 \times 10^3 \times 20 \times 10^{-6} = 0.4$$

$$V_o = -\frac{1}{RC} \int_0^t v_i dt$$

$$\begin{aligned} V_o &= -\frac{1}{RC} \left[\frac{V_i}{j\omega} + \pi V_i(0) \delta(\omega) \right] \\ &= -\frac{1}{0.4} \left[\frac{2}{j\omega(2 + j\omega)} + \pi \delta(\omega) \right] \end{aligned}$$

$$I_o = \frac{V_o}{20} mA = -0.125 \left[\frac{2}{j\omega(2 + j\omega)} + \pi \delta(\omega) \right]$$

$$= -\frac{0.125}{j\omega} + \frac{0.125}{2 + j\omega} - 0.125\pi \delta(\omega)$$